
CS223-5: Digital Design Project Can Avşar 21902111 December 25, 2020

 
# 1) Block Diagram of Controller/Datapath



I used some mux and they are connected to some inputs and outputs. I only showed the controller and the datapath. Also clock is going to the datapath and led's are determined by the datapath.

It is a bit confusing because of there are only controller and datapath, the report wanted the controller/datapath diagram.

# 2) State Diagram of the Controller

 

I used 6 states on my controller and they are wait, store, load, add, branch (if equals) and stop. Each one has different operation codes and when the controller receives the instruction, the operation code which is the first 3 bits of the instruction, determines the next state.

Also, there are some variables and their conditions under each state. These are the details of this diagram. Note: The photo is a bit pale but I hope they are readable.

# 3) SystemVerilog Code Implementation of Single Cycle Processor and Buttons

I will include all codes with the .zip file but there are some initial codes for the processor.

## Top Design:

```
module TopDesign
  input logic clk,
  input logic [15:0] swlns,
  input logic [4:0] debouncer,
  output logic [15:0] insLed,
  output logic [6:0]seg,
  output logic dp,
  output logic[3:0] an
  );
  logic previous, next, getFromSwitches, getFromMemory, reset;
  logic branch, stop, add;
  logic [7:0] data1;
  logic [3:0] data2;
  logic registerWriteEnable;
  logic [3:0] writeRegisterAddress;
  logic [7:0] readRegisterData1, readRegisterData2, writeRegisterData;
  logic [4:0] romMemoryAddress = 5'b00000;
  logic [15:0] instruction;
  logic [15:0] romMemoryInstruction;
  logic memoryWriteEnable;
  logic [3:0] writeDataAddress;
  logic [3:0] memoryAddress = 4'b0000;
  logic [7:0] readRamData1, readRamData2, writeData;
  logic [2:0] aluControl;
  logic [7:0] aluResult;
  // create buttons
  Debouncer upButton( clk, debouncer[1], reset);
  Debouncer centerButton(clk, debouncer[0], getFromSwitches);
  Debouncer rightButton(clk, debouncer[3], next);
  Debouncer leftButton(clk, debouncer[2], previous);
```

```
Debouncer downButton(clk, debouncer[4], getFromMemory);
always_ff@(posedge clk, posedge reset)
begin
  if (reset)
    begin
    romMemoryAddress <= 5'b00000;
    end
  else begin
  if (!stop)
  begin
  instruction <= 16'b1000000000000000;
    if (previous)
       if (memoryAddress == 4'b0000)
         memoryAddress <= 4'b1111;
       else
         memoryAddress <= memoryAddress - 1;
    else if (next)
        if (memoryAddress == 4'b1111)
          memoryAddress <= 4'b0000;
        else
          memoryAddress <= memoryAddress + 1;
     else if (getFromMemory)
       begin
       instruction <= romMemoryInstruction;</pre>
       if (romMemoryAddress == 5'b11111)
         romMemoryAddress <= 5'b00000;
       else
         romMemoryAddress <= romMemoryAddress + 1;
    end
    else if (getFromSwitches)
       instruction <= swlns;
    else if (branch)
       romMemoryAddress <= instruction[12:8];</pre>
  end
  end
end
```

Controller controlUnit( reset, instruction[15:13], stop, add, branchEnable, registerWriteEnable, memoryWriteEnable, aluControl);

```
Multiplexer multiplexer1(instruction[12], readRegisterData1, instruction[7:0], writeData); Multiplexer multiplexer2(instruction[12], readRamData1, instruction[7:0], data1); Multiplexer multiplexer3(add, data1, aluResult, writeRegisterData);
```

MultiplexerBranch multiplexer4(branchEnable, 0, aluResult[0], branch);

MultiplexerAddress multiplexer5(instruction[12], instruction[7:4], instruction[11:8], writeDataAddress);

MultiplexerAddress multiplexer6(instruction[12], instruction[7:4], instruction[11:8], data2); MultiplexerAddress multiplexer7(add, data2, instruction[11:8], writeRegisterAddress);

DataMemory memory(clk, reset, memoryWriteEnable, writeDataAddress, writeData, instruction[3:0], memoryAddress, readRamData1, readRamData2);

In struction Memory instructions (rom Memory Address, rom Memory Instruction, in sLed);

ALU alu(readRegisterData1, readRegisterData2, aluControl, aluResult);

RegisterFile registerFile(clk, reset, registerWriteEnable, writeRegisterAddress, writeRegisterData, instruction[3:0], instruction[7:4], readRegisterData1, readRegisterData2);

SevenSegmentDisplay sevenSegmentDisplay(clk, memoryAddress, 1, readRamData2[7:4], readRamData2[3:0], seg, dp, an);

endmodule

#### Controller:

```
module Controller(
  input logic reset,
  input logic [2:0] operationCode,
  output logic stop, add, branch, registerWriteEnable, memoryWriteEnable,
  output logic [2:0] aluControl);
  always comb
  begin
     if( reset)
     begin
       add = 0;
       branch = 0;
       stop = 0;
       memoryWriteEnable = 0;
       registerWriteEnable = 0;
       aluControl = 3'b000;
     end
     else begin
```

```
case(operationCode)
  3'b000: // store
  begin
     add = 0;
     branch = 0;
     stop = 0;
     memoryWriteEnable = 1;
     registerWriteEnable = 0;
     aluControl = 3'b000;
  end
  3'b001: //load
  begin
     add = 0;
     branch = 0;
     stop = 0;
     memoryWriteEnable = 0;
     registerWriteEnable = 1;
     aluControl = 3'b001;
  end
  3'b010: // add
  begin
     add = 1;
     stop = 0;
     branch = 0;
     memoryWriteEnable = 0;
     registerWriteEnable = 1;
     aluControl = 3'b010;
  end
  3'b101: // branch if equals
  begin
     add = 0;
     stop = 0;
     branch = 1;
     memoryWriteEnable = 0;
     registerWriteEnable = 0;
     aluControl = 3'b101;
  end
  3'b111: // stop
  begin
     add = 0;
     stop = 1;
     branch = 0;
     memoryWriteEnable = 0;
     registerWriteEnable = 0;
```

```
aluControl = 3'b000;
end

default:
begin
add = 0;
stop = 0;
branch = 0;
memoryWriteEnable = 0;
registerWriteEnable = 0;
aluControl = 3'b000;
end
endcase
end
end
endmodule
```

## Multiplexer:

```
module Multiplexer(
input logic controllnput,
input logic [7:0] a, b,
output logic [7:0] out);

always_comb
begin
case (controllnput)
0: out = a;
1: out = b;
endcase
end
endmodule
```

## ALU:

```
module ALU(
input logic [7:0] a,
input logic [7:0] b,
input logic [2:0] aluControl,
output logic [7:0] aluResult);
always_comb
begin
case(aluControl)
3'b000: aluResult = 0;
```

```
3'b001: aluResult = 0;
3'b010: aluResult = a + b;
3'b101: aluResult = ~(a ^ b); // xnor
3'b111: aluResult = 0;
default: aluResult = 0;
endcase
end
endmodule
```

## Data Memory:

```
module DataMemory(
input logic clk,
input logic reset,
input logic writeEnable,
input logic [3:0] writeAddress,
input logic [7:0] writeData,
input logic [3:0] readAddress1,
input logic [3:0] readAddress2,
output logic [7:0] readData1,
output logic [7:0] readData2);
logic [7:0] mem [15:0];
always_ff @(posedge clk)
  begin
  if(reset) begin
          mem[0] \le 8'b0;
          mem[1] \le 8'b0;
          mem[2] \le 8'b0;
          mem[3] \le 8'b0;
          mem[4] \le 8'b0;
          mem[5] \le 8'b0;
          mem[6] \le 8'b0;
          mem[7] \le 8'b0;
          mem[8] \le 8'b0;
          mem[9] \le 8'b0;
          mem[10] \le 8'b0;
          mem[11] \le 8'b0;
          mem[12] <= 8'b0;
          mem[13] \le 8'b0;
          mem[14] <= 8'b0;
          mem[15] <= 8'b0;
      end
  else
     if (writeEnable == 1)
     mem[writeAddress] <= writeData;
  end
  assign readData1 = mem[readAddress1];
```

endmodule

## Register File:

```
module RegisterFile(
input logic clk,
input logic reset,
input logic regWriteEnable,
input logic [3:0] regWriteAddress,
input logic [7:0] regWriteData,
input logic [3:0] regReadAddress1,
input logic [3:0] regReadAddress2,
output logic [7:0] regReadData1,
output logic [7:0] regReadData2);
   logic [7:0] regMem[15:0];
   always_ff@ (posedge clk, posedge reset) begin
     if(reset)
       begin
          regMem[0] <= 8'b0;
          regMem[1] <= 8'b0;
          regMem[2] <= 8'b0;
          regMem[3] <= 8'b0;
          regMem[4] <= 8'b0;
          regMem[5] <= 8'b0;
          regMem[6] <= 8'b0;
          regMem[7] <= 8'b0;
          regMem[8] <= 8'b0;
          regMem[9] <= 8'b0;
          regMem[10] <= 8'b0;
          regMem[11] <= 8'b0;
          regMem[12] <= 8'b0;
          regMem[13] <= 8'b0;
          regMem[14] <= 8'b0;
          regMem[15] <= 8'b0;
      end
      else
       begin
          if(regWriteEnable == 1)
            begin
             regMem[regWriteAddress] <= regWriteData;</pre>
          end
      end
      end
```

```
assign regReadData1 = regMem[regReadAddress1];
assign regReadData2 = regMem[regReadAddress2];
endmodule
```

## Instruction Memory:

```
module InstructionMemory(
input logic [4:0] readAddress,
output logic [15:0] readData, readData2);
logic [15:0] rom[31:0];
always_comb
   begin
    rom[0] = 16'b001_0_0000_00000000;
    rom[1] = 16'b001 0 0000 00010001;
    rom[2] = 16'b001_1_0010_00000000;
    rom[3] = 16'b001 1 0011 00000000;
    rom[4] = 16'b001_1_0100_00000001;
    rom[5] = 16'b101_0_1001_00100001;
    rom[6] = 16'b010_0_0011_00110000;
    rom[7] = 16'b010 0 0010 00100100;
    rom[8] = 16'b101 \ 0 \ 0101 \ 0000 \ 0000;
    rom[9] = 16'b000_0_0000_0011_0011;
    rom[10] = 16'b001_0_0000_00000000;
    rom[11] = 16'b001 0 0000 00010001;
    rom[12] = 16'b001_1_0010_00000000;
    rom[13] = 16'b001_1_0011_00000000;
    rom[14] = 16'b001_1_0100_00000001;
    rom[15] = 16'b101_0_1001_00100001;
    rom[16] = 16'b010_0_0011_00110000;
    rom[17] = 16'b010_0_0010_00100100;
    rom[18] = 16'b101_0_0101_0000_0000;
    rom[19] = 16'b000 0 0000 0011 0011;
    rom[20] = 16'b010_x_1100_1000_1001;
    rom[21] = 16'b010_x_1101_1010_1011;
    rom[22] = 16'b101 00110 1000 1101;
    rom[23] = 16'b101 00010 1001 1011;
    rom[25] = 16'b101 xxxxxxxxxxxxx;
    rom[26] = 16'b101_xxxxxxxxxxxxxxx;
    rom[28] = 16'b011 xxxxxxxxxxxxx;
    rom[30] = 16b101 xxxxxxxxxxxxxxx;
    rom[31] = 16b111_xxxxxxxxxxxxxx;
```

end

assign readData = rom[readAddress];
assign readData2 = rom[readAddress+1];
endmodule